

NEW TEXTILES

LEDs & TEXTILE CIRCUITS

MAS 963, E14-525


Professor: Leah Buechley

TA: Hannah Perner-Wilson


Wednesdays 1-4pm and Fridays 2-3pm

<http://newtextiles.media.mit.edu/>


a simple circuit...

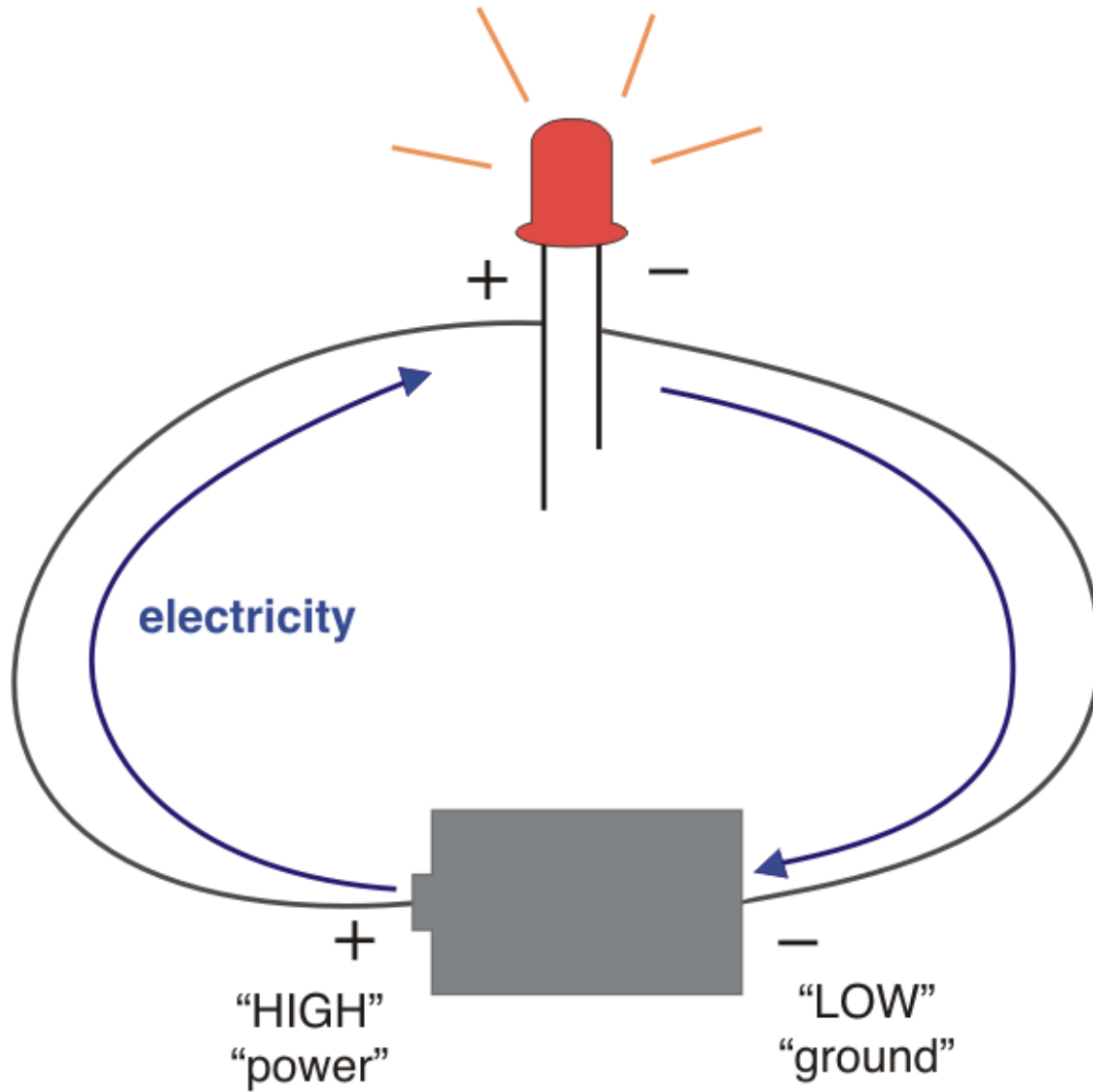

a simple circuit...with a switch

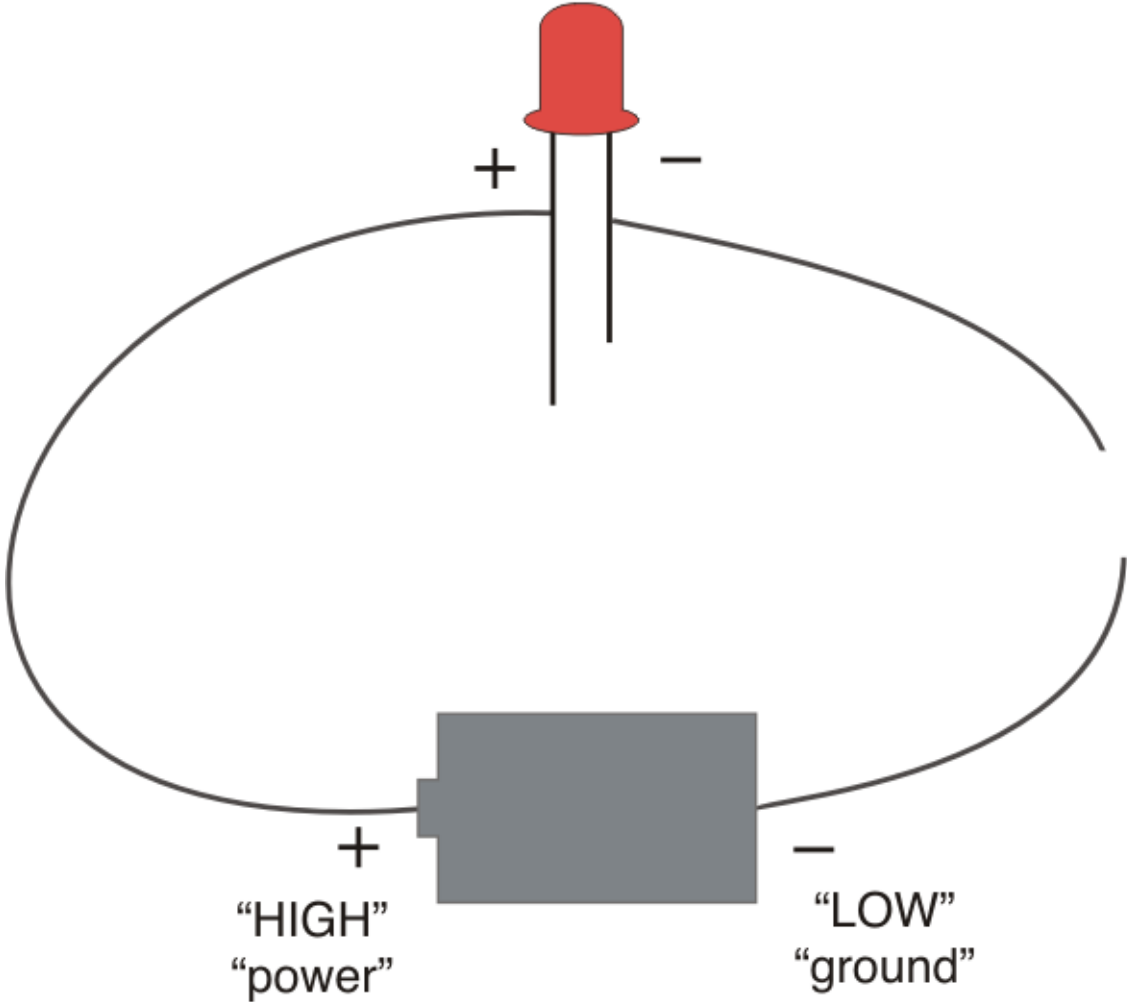


a simple circuit...with a switch

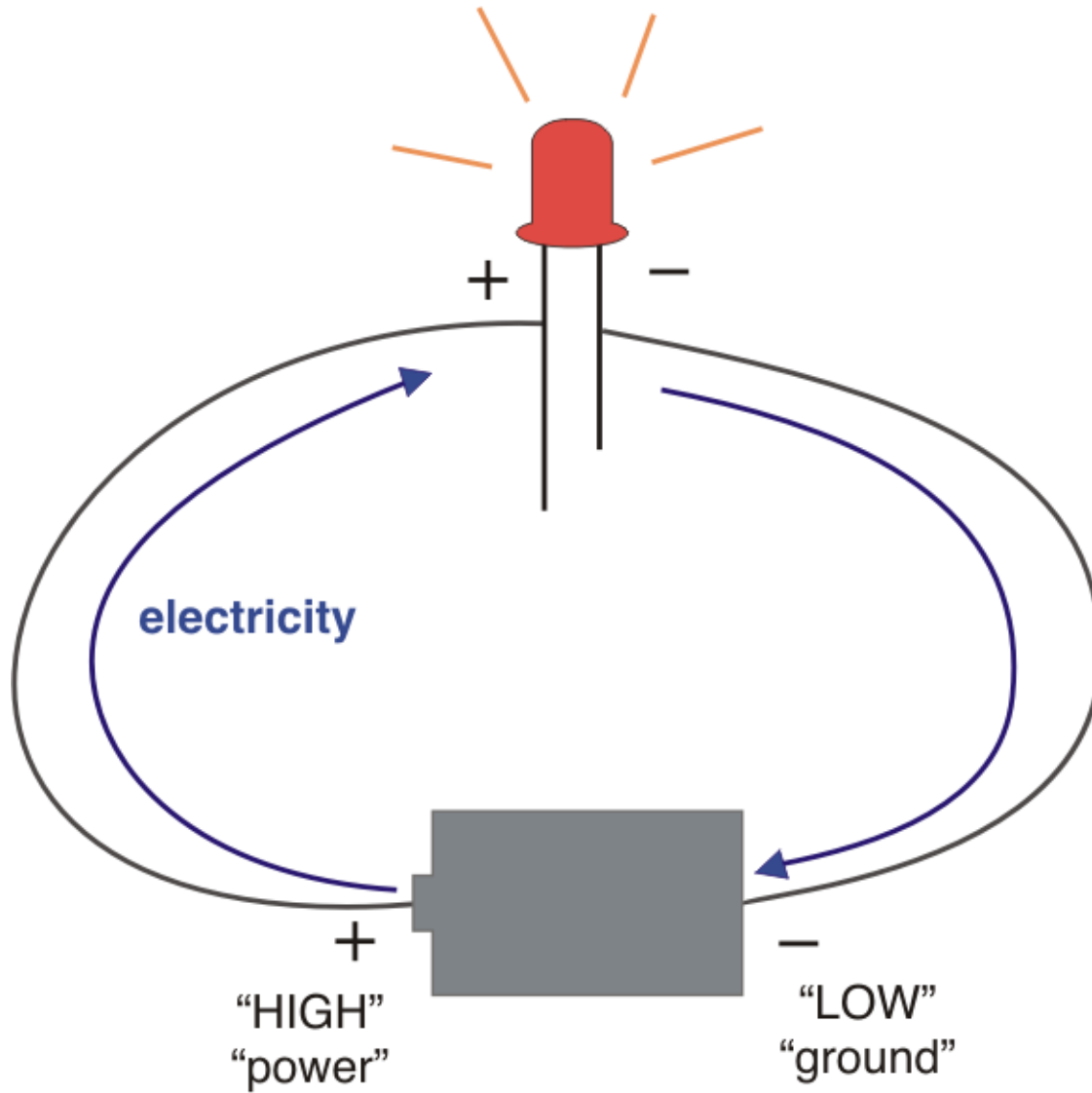


LEDs






LEDs, telling + from -

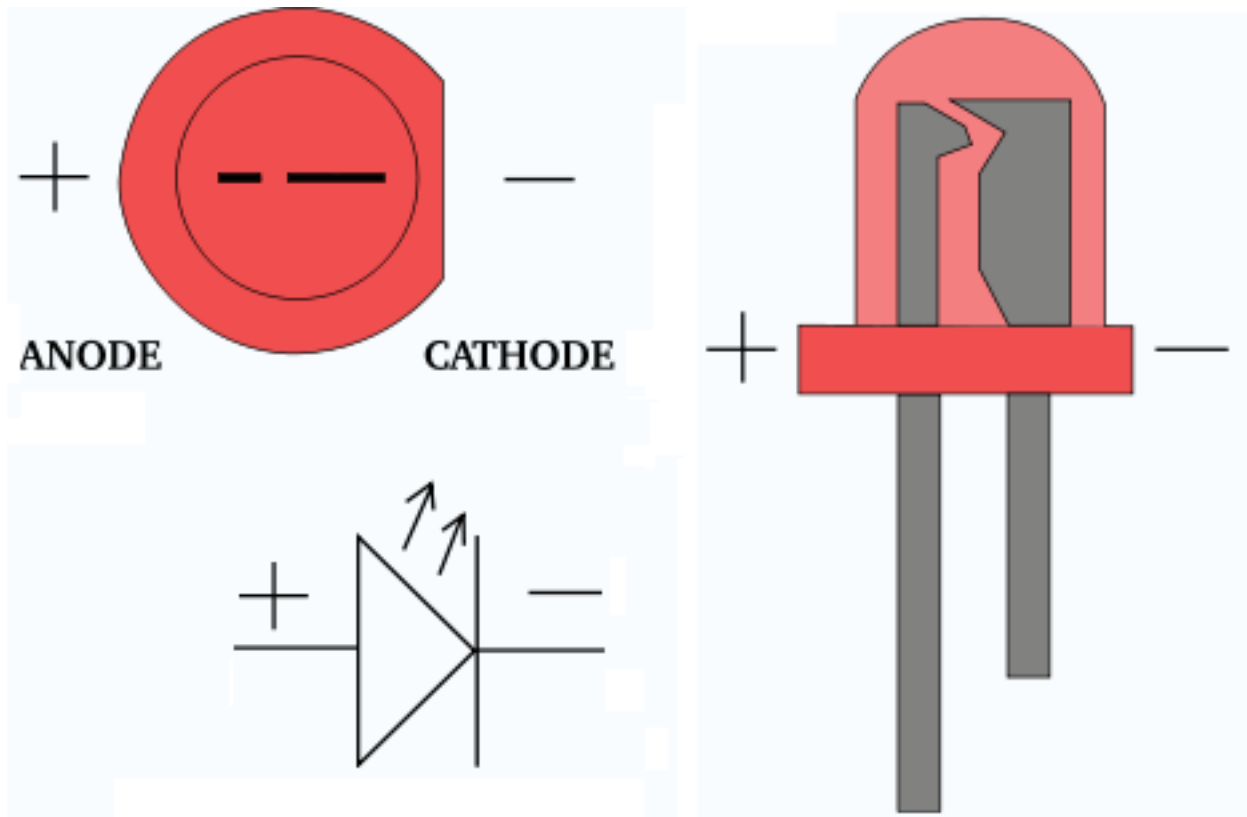

Making LEDs Sewable

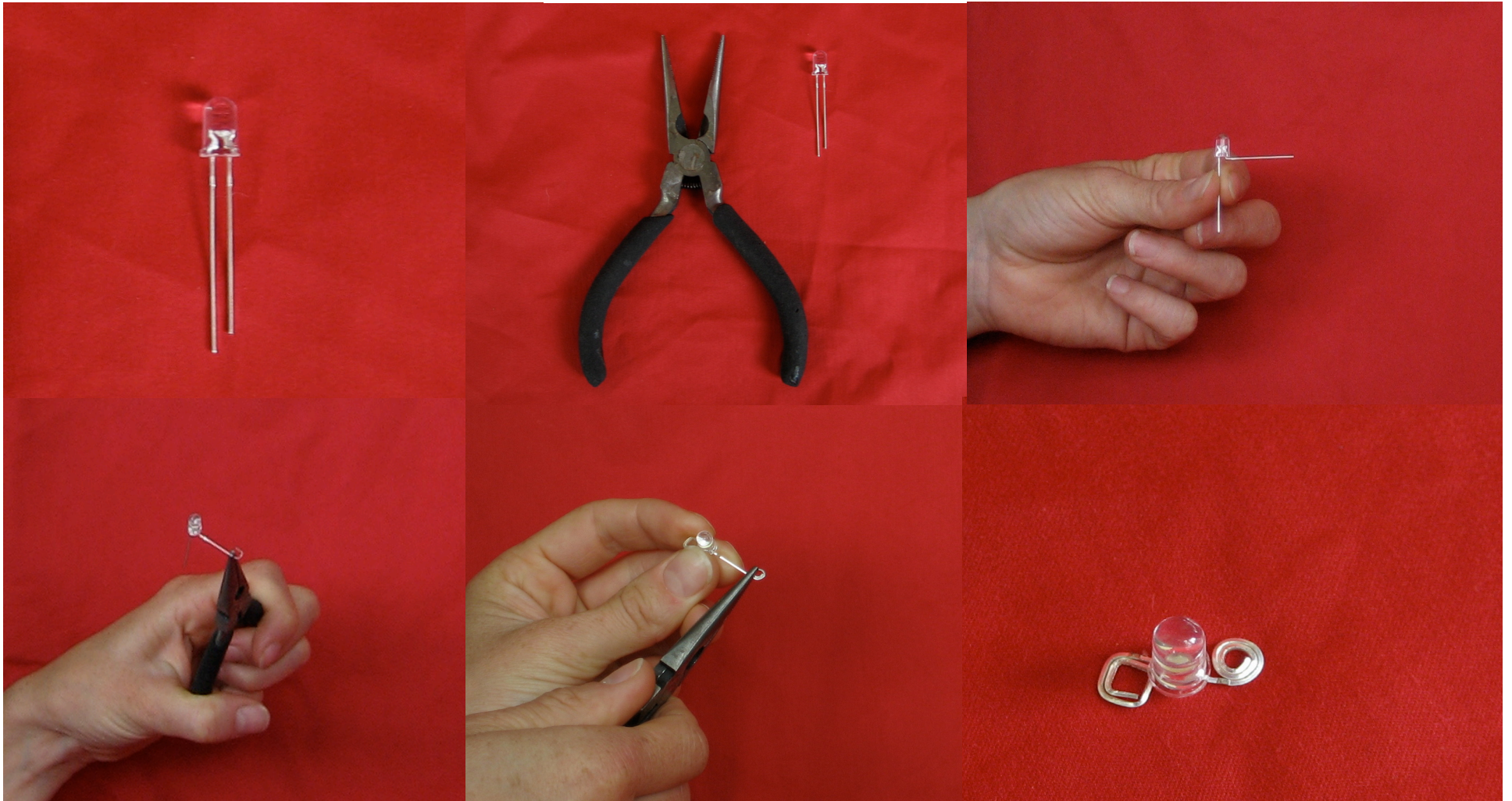

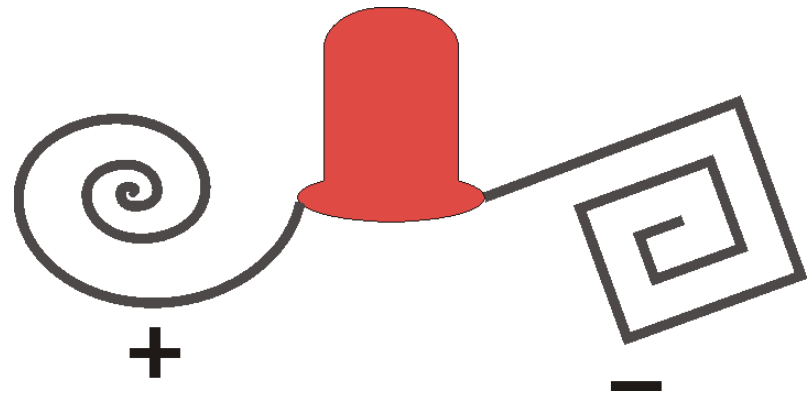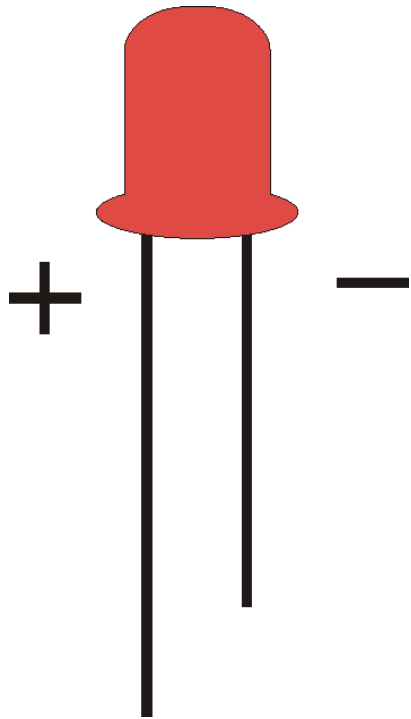

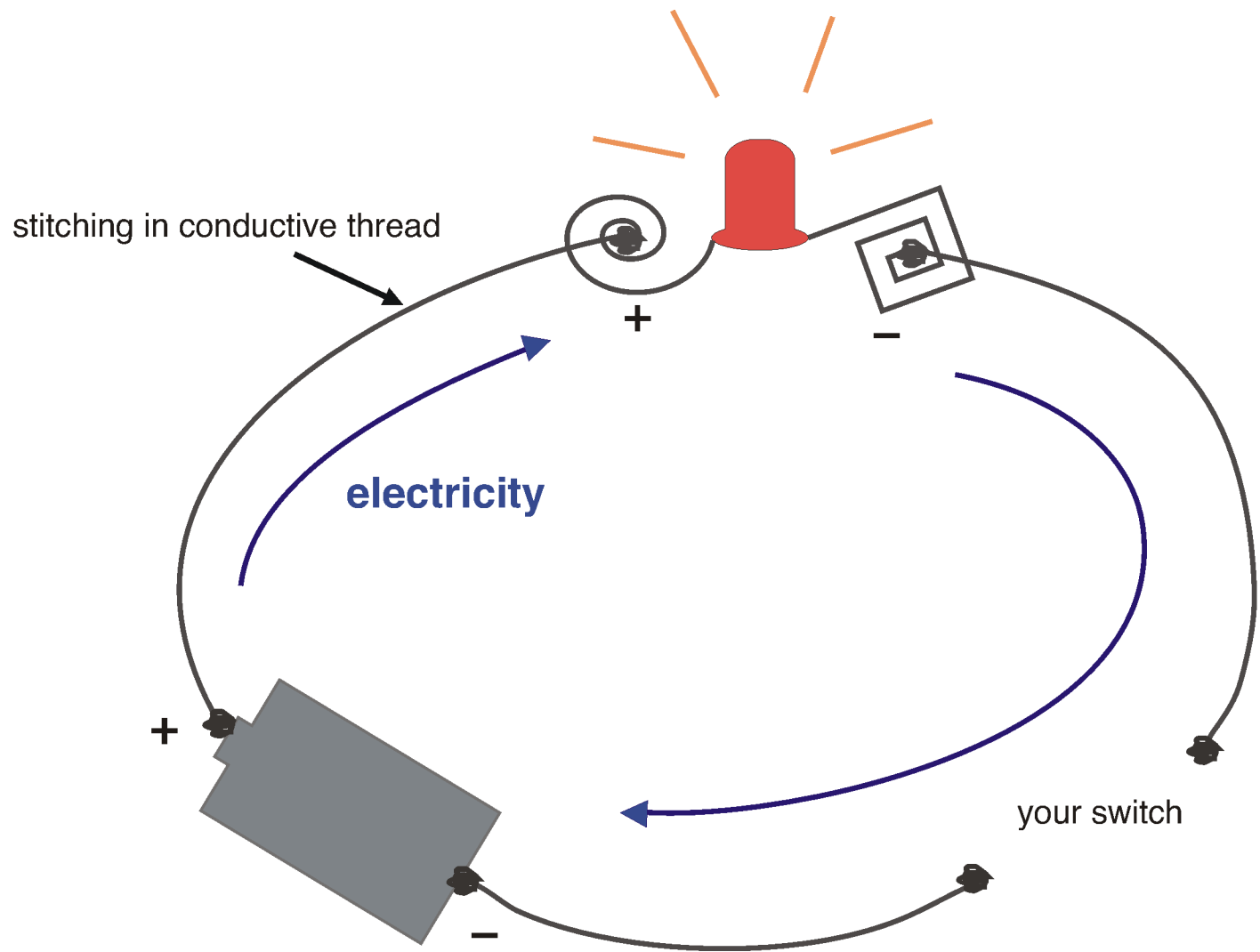

stitching in conductive thread

+

-

electricity

+

-

your switch